

Student ID: _____

CS 151 Quiz 1

Name : _____ , _____
(Last Name) (First Name)

Student ID : _____

Signature : _____

Instructions:

1. Please verify that your paper contains **8 pages** including this cover.
2. Write down your Student-Id on the top of each page of this quiz.
3. This exam is **closed book**. No notes or other materials are permitted.
4. Total credits of this midterm are **50 points**.
5. To receive full credits, you must show your work clearly.
6. **No re-grades will be entertained if you use a pencil.**
7. Calculators are **NOT** allowed.

Student ID: _____

Q1: [Data Conversion] _____ [9 points]

(a)- Convert the following decimal number to binary using divide-by-2 method: (3 points)

232

$$232/2 = 116/2 = 58/2 = 29/2 = 14/2 = 7/2 = 3/2 = 1$$

Remainder: 0 0 0 1 0 1 1

$$\Rightarrow 232_{10} = 11101000_2$$

(b)- Convert the following binary number to decimal: (3 points)

1 0 1 0 1 1 1 0

$$\begin{aligned} 10101110 &= 1*2^7 + 0*2^6 + 1*2^5 + 0*2^4 + 1*2^3 + 1*2^2 + 1*2^1 + 0*2^0 \\ &= 128 + 32 + 8 + 4 + 2 \\ &= 174_{10} \end{aligned}$$

(c)- Convert the following hexadecimal number to binary: (3 points)

C1F

$$C1F_{16} = (1100\ 0001\ 1111)_2$$

Student ID: _____

Q2: [Combinational Logic Design] [10 points]

A binary adder has two inputs $A = a_1a_0$ and $B = b_1b_0$ and two outputs $S = s_1s_0$ and C_{out} which is the carry out of the adder saying if $a_1 + b_1$ generates a carry. Using truth table write the equation for output C_{out} .

You are NOT needed to simplify the function.

NOTE: The truth table has 4 inputs and one output.

a_1	a_0	b_1	b_0	C_{out}
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$C_{out} = a_1'a_0b_1b_0 + a_1a_0'b_1b_0' + a_1a_0'b_1b_0 + a_1a_0b_1'b_0 + a_1a_0b_1b_0' + a_1a_0b_1b_0$$


Student ID: _____

Q3: [Mux/Decoder application]

[15 points]


(a) For function $F(a,b,c) = a'bc + ab'c' + abc + ab'c + a'b'c'$:
Implement F by means of a 4-to-1 multiplexer. You should not simplify the function.
(8 points)

(HINT: You can use NOT gates to invert the input to the MUX)

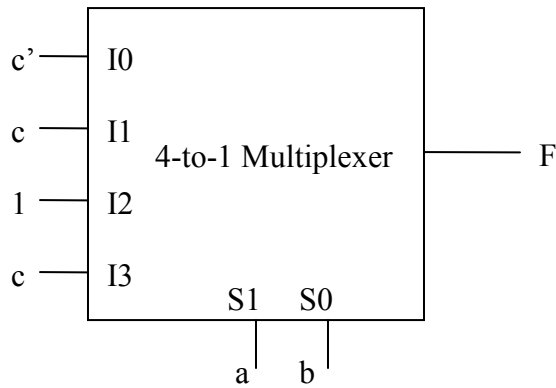

Student ID: _____

- (b) For the same function $F(a,b,c) = a'bc + ab'c' + abc + ab'c + a'b'c'$:
Implement F by means of a 3-to-8 decoder. You should not simplify the function.
(7 points)

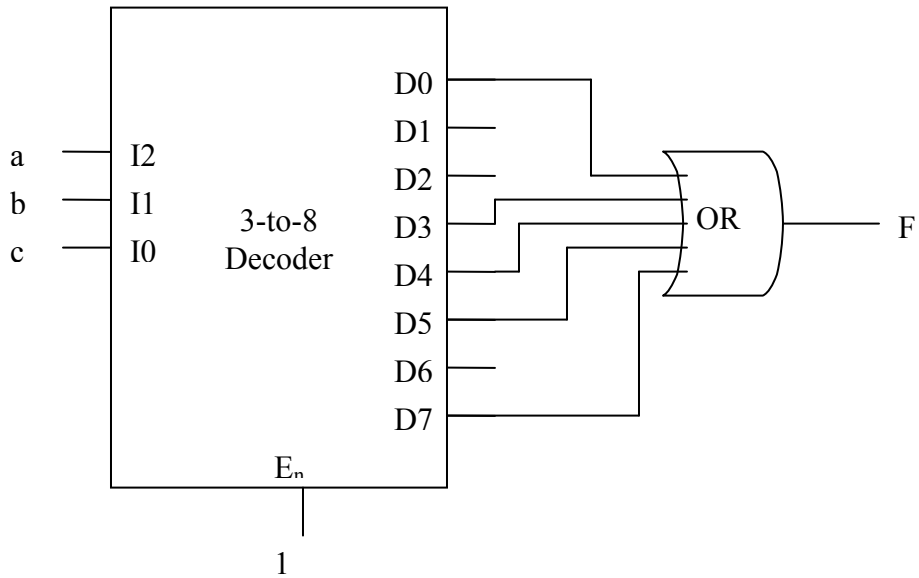

Student ID: _____

Q4: [Combinational Logic Design] _____ [5 points]

A network router connects multiple computers together and allows them to send messages to each other. If two or more computers send messages simultaneously, they collide and the messages must be resent. Create a collision detection circuit for a router that connects 3 computers. The circuit has 3 inputs labeled M0, M1 and M2 that are 1 when the corresponding computer is sending a message and 0 otherwise. The circuit has one output labeled C that is 1 when a collision is detected and 0 otherwise. Write the equation for C.

$$C = M_2M_1M_0' + M_2M_1'M_0 + M_2'M_1M_0 + M_2M_1M_0$$

Student ID: _____

Q5: [Boolean algebra] _____ [11 points]

(a) Prove the following Boolean equation using Boolean algebra: (6 points)

$$\mathbf{a(a + b + c)(a' + b + c')(a + b + c')(a' + b'c) = 0}$$

$$\left. \begin{array}{l} (a + b + c)(a + b + c') = a + b + c.c' = a + b \\ (a' + b + c')(a' + b'c) = a' + b'c(b + c') = a' \end{array} \right\} \Rightarrow a(a + b)a' = 0$$

Student ID: _____

(b) Use algebraic manipulation to convert the following equation to sum-of-product form: (5 points)

$$x(y+z)(w) + x(y+w)' + y(xz)'$$

$$xyw + xzw + x(y'w') + y(x' + z') = \underline{xyw + xzy + xy'w' + yx' + yz'}$$