

3.2(b,c)

b) $1/100,000,000 = 10 \text{ ns}$


c) $1/1,500,000,000 = 0.66 \text{ ns} = 667 \text{ ps}$

3.4(a,d)


a) $1/500\text{ms} = 2 \text{ Hz}$

d) $1/20\text{ps} = 50,000,000,000 \text{ Hz} = 50 \text{ GHz}$


3.9

 


3.11

 


3.13

 

3.15

 


3.21

 


3.23

Inputs: X, Outputs: Y

 


3.27

Inputs: B, Outputs: s1,s0

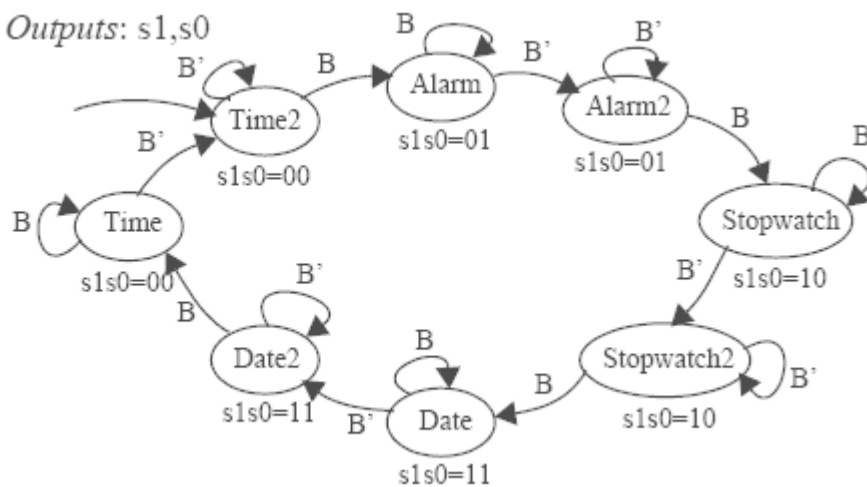


3.28

Inputs: B,R, Outputs: s1,s0

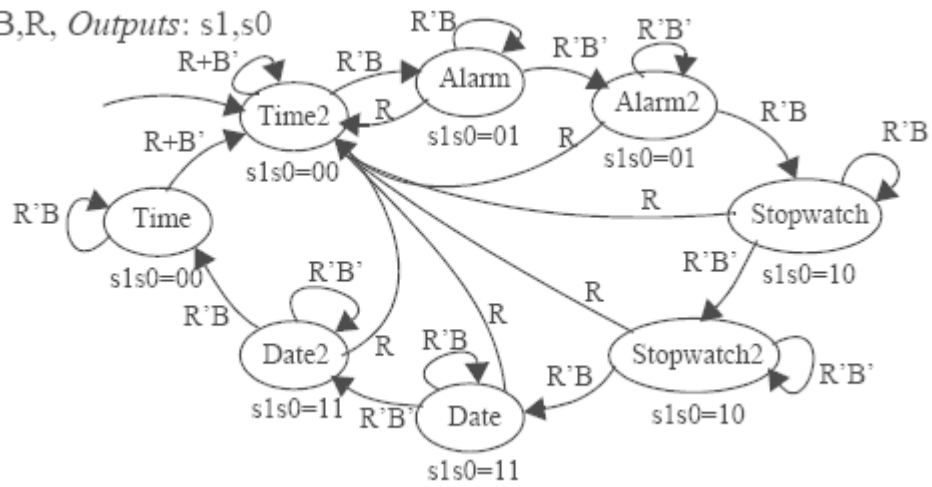


3.29

Inputs: gcnt
Outputs: x, y, z

 

3.30

 

3.32


- a) 2 bits
- b) 3 bits
- c) 4 bits
- d) 5 bits
- e) 10 bits

3.39

Step 1 - Capture the FSM

The appropriate FSM is given above.

Step 2 - Create the architecture

 

Step 3 - Encode the states

A straightforward encoding is A=00, B=01, C=10, D=11.

Step 4 - Create the state table

Inputs Outputs
s1 s0 a b n1 n0 y

0 0 0 0 1 0 0

0 0 0 1 0 1 0

0 0 1 0 0 0 0

0 0 1 1 0 0 0

0 1 0 0 0 1 1

0 1 0 1 0 1 1

0 1 1 0 1 0 1

0 1 1 1 1 0 1

1 0 0 0 1 0 1

1 0 0 1 1 1 1

1 0 1 0 1 0 1

1 0 1 1 1 1 1

1 1 0 0 0 0 0

1 1 0 1 0 0 0

1 1 1 0 0 0 0

1 1 1 1 0 0 0

Step 5 - Implement the combinational logic

$$n1 = s1's0'a'b' + s1's0a + s1s0'$$

$$n0 = s1's0'a'b + s1's0a' + s1s0'b$$


$$y = s1's0 + s1s0'$$

Note: The above equations can be minimized further.

3.41


Step 1 - Capture the FSM

Inputs: B, Outputs: s1,s0

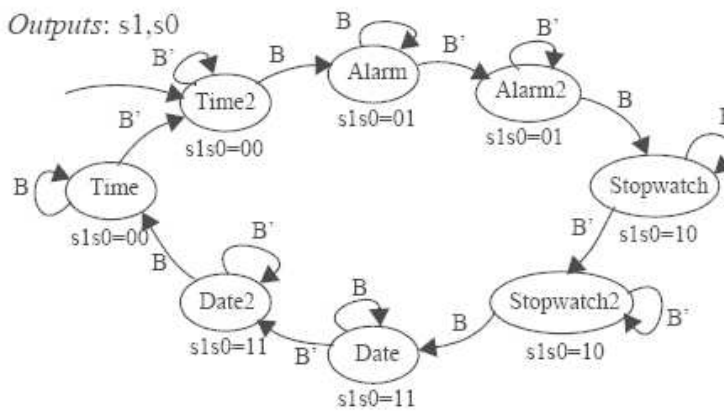

The FSM was created during Exercise 3.27.

Step 2 - Create the architecture

 

Step 3 - Encode the states

A straightforward encoding is Time2=000, Alarm=001, Alarm2=010, Stopwatch=011, Stopwatch2=100, Date=101, Date2=110, Time=111.

Step 4 - Create the state table

Inputs				Outputs				
s2	s1	s0	B	n2	n1	n0	s1	s0
0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0
0	0	1	0	0	1	0	0	1
0	0	1	1	0	0	1	0	1
0	1	0	0	0	1	0	0	1
0	1	0	1	0	1	1	0	1
0	1	1	0	1	0	0	1	0
0	1	1	1	0	1	1	1	0
1	0	0	0	1	0	0	1	0
1	0	0	1	1	0	1	1	0
1	0	1	0	1	0	1	1	1
1	0	1	1	1	1	0	1	1
1	1	0	0	1	1	0	1	1
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0
1	1	1	1	1	1	1	0	0

Step 5 - Implement the combinational logic

$$n2 = s2's1s0B' + s2s1' + s2s0' + s2B$$

$$n1 = s1s0' + s1B + s2s0B + s2's1's0B'$$

$$n0 = s0'B + s2'B + s1B + s2s1's0B'$$


$$s1 = s2s0' + s2s1' + s2's1s0$$

$$s0 = s1 \text{ XOR } s0$$

3.42


Step 1 - Capture the FSM

Inputs: gcnt
Outputs: x, y, z

 

The FSM was created during Exercise 3.29.

Step 2 - Create the architecture

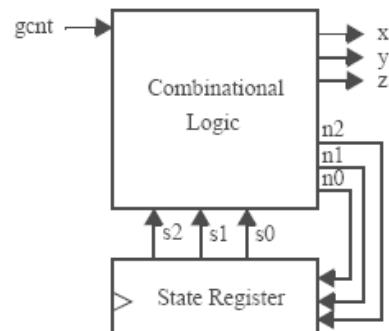

Step 3 - Encode the states

A straightforward encoding is A=000, B=001, C=010, D=011, E=100, F=101, G=110, H=111.

Step 4 - Create the state table

		Inputs				Outputs					
		s2	s1	s0	gcnt	n2	n1	n0	x	y	z
A		0	0	0	0	0	0	0	0	0	0
		0	0	0	1	0	0	1	0	0	0
B		0	0	1	0	0	0	1	0	1	0
		0	0	1	1	0	1	0	0	1	0
C		0	1	0	0	0	1	0	0	1	1
		0	1	0	1	0	1	1	0	1	1
D		0	1	1	0	0	1	1	0	0	1
		0	1	1	1	1	0	0	0	0	1
E		1	0	0	0	1	0	0	1	0	1
		1	0	0	1	1	0	1	1	0	1
F		1	0	1	0	1	0	1	1	1	1
		1	0	1	1	1	1	0	1	1	1
G		1	1	0	0	1	1	0	1	1	0
		1	1	0	1	1	1	1	1	1	0
H		1	1	1	0	1	1	1	1	0	0
		1	1	1	1	0	0	0	1	0	0

Step 5 - Implement the combinational logic

$$n2 = s2's1s0gcnt + s2s1' + s2s1s0' + s2s1s0gcnt'$$

$$n1 = s2's1's0gcnt + s2's1s0' + s2's1s0gcnt' + s2s1's0gcnt + s2s1s0' + s2s1s0gcnt'$$

$$n0 = s2's1's0'gcnt + s2's1's0gcnt' + s2's1s0'gcnt + s2's1s0gcnt' + s2s1's0'gcnt + s2s1's0gcnt' + s2s1s0'gcnt + s2s1s0gcnt'$$

$$x = s2$$

$$y = s2's1's0 + s2's1s0' + s2s1's0 + s2s1s0'$$

$$z = s2's1 + s2s1'$$


Note: The above equations can be minimized further.

3.45

If we AND each pair of transitions with each other in state A, we notice one pair does not evaluate to 0: $a \cdot a' \cdot b$. This shows that more than one condition can be true simultaneously.

Furthermore, if we OR all the conditions from state C, we notice that the expression does not evaluate to 1: b . This shows that there may be a combination of inputs in which one condition from state C is not true.

 We can address both of these problems with the following changes:



3.48

