
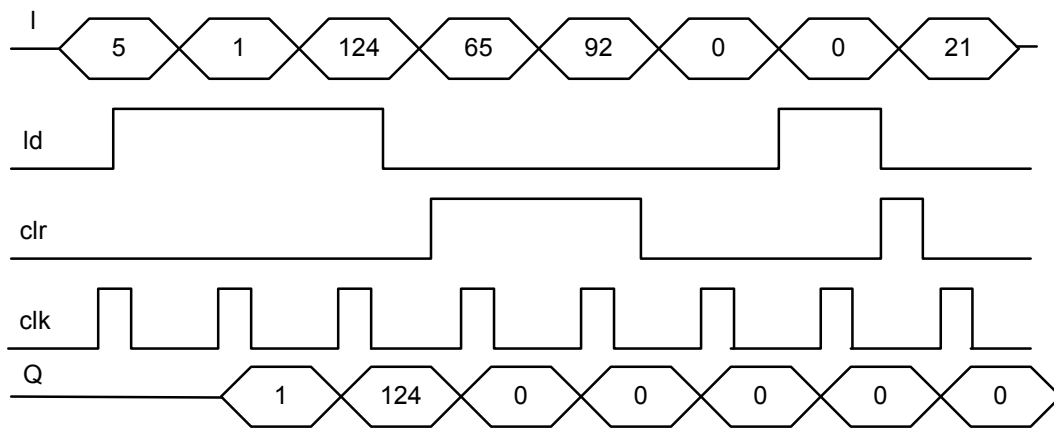


4.2

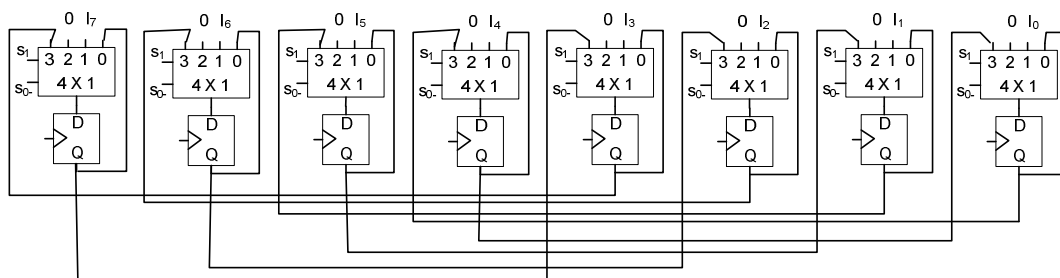

4.5




4.8

An 8-bit carry-ripple adder contains 7 full adders and 1 half adder. Each full adder requires 2 gate delays and the half adder requires 1 gate delay. Therefore a minimum of $(7 \text{ FA} * 2 \text{ gate delay/FA} + 1 \text{ HA} * 1 \text{ gate delay/HA}) * 1\text{ns/gate delay} = 15\text{ns}$ is required to ensure that the carry-ripple adder's sum is correct.


4.10

10-bit carry ripple adder

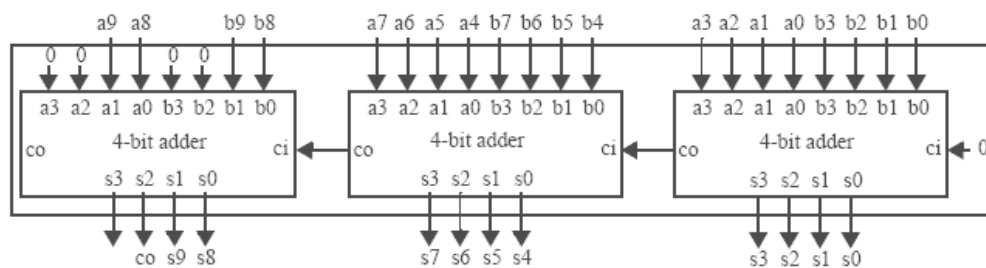


4.12

$$A+B+C+D = ((A+B) + (C+D))$$

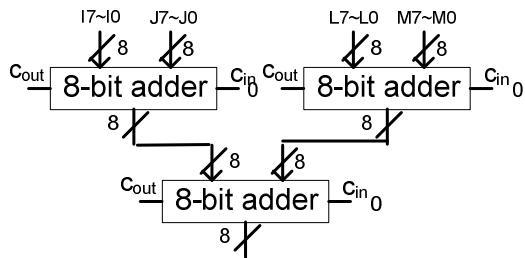


4.13

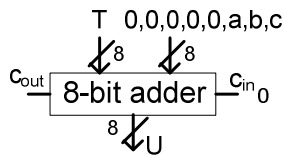


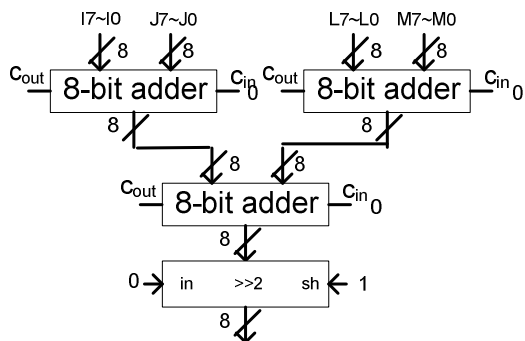4.17

'Divide by four' means 2 right shifts in binary system.



4.20

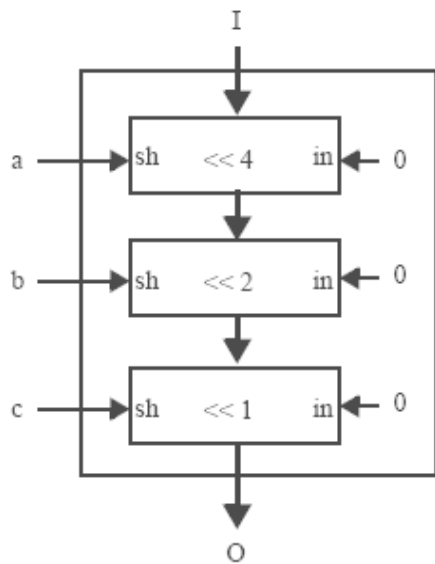


4.26

For each 1-bit comparator, assuming gte means “a is gte b” and lte means “a is lte b”,


$gte = igte((a \text{ XNOR } b) + ab')$,

$lte = ilte((a \text{ XNOR } b) + a'b)$.

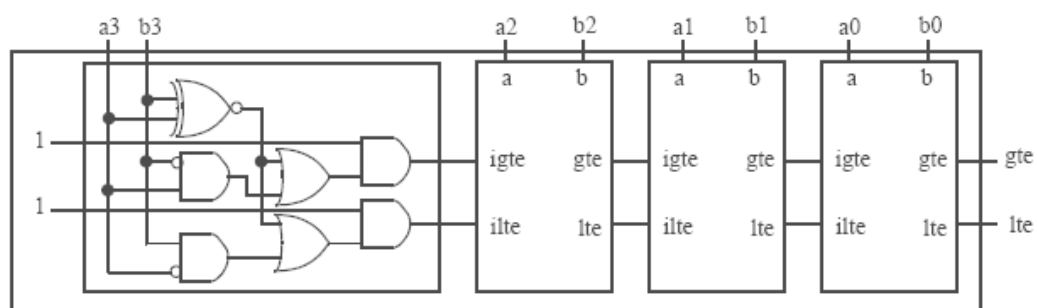“igte” and “ilte” are the result of comparison for higher bits:



4.29

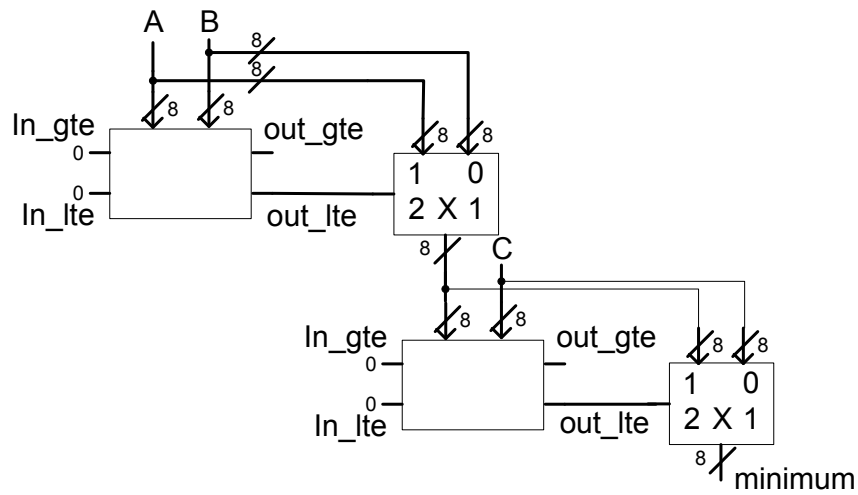


4.48


(d) $11000000 \rightarrow 2'$ complement $01000000 = 2^6 = 64$
 $(11000000)_2 = -64$

4.51


(f) $125 = 128 - 3 = 2^7 - 3 = 010000000 - 011 = 01111101$
 Therefore, -125 is 10000011 in two's complement form

4.54

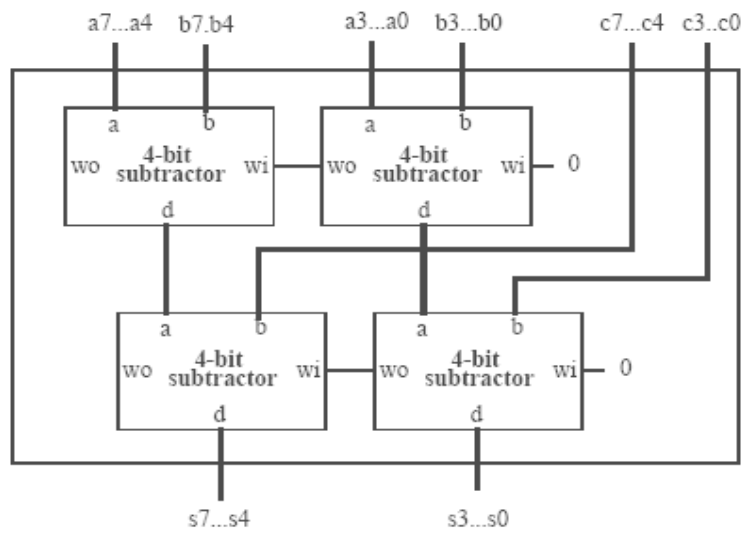
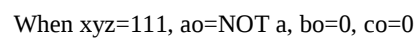
$$(273)_{10} = (\underline{111})_{16}$$


4.58

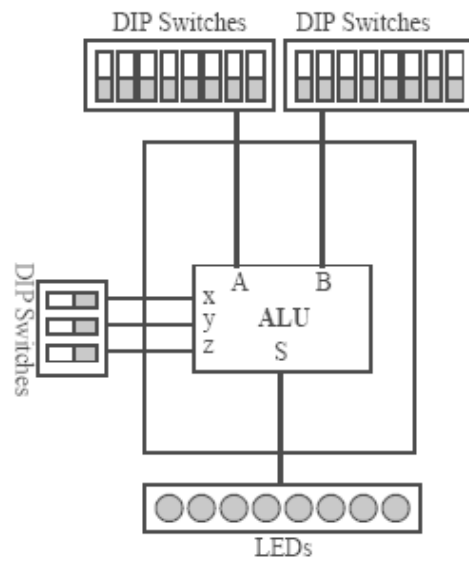

4.60

